

# Electronics Lab Course

## Experiment #0: Introduction and Preparational Experiment

Christopher Jörn

April 12, 2015

### Contents

<b>1</b>	<b>Aims of the experiment</b>	<b>2</b>
<b>2</b>	<b>Preperational exercises</b>	<b>3</b>
2.1	0.2.1.A . . . . .	3
2.2	0.2.1.B . . . . .	3
2.3	0.2.2.C . . . . .	3
	2.3.1 0.2.2.C.1 . . . . .	3
	2.3.2 0.2.2.C.2 . . . . .	4
2.4	0.3.3.E . . . . .	4
<b>3</b>	<b>Procedure</b>	<b>5</b>
3.1	0.4.1.a . . . . .	5
3.2	0.4.1.b . . . . .	5
<b>4</b>	<b>Measurement</b>	<b>6</b>
4.1	0.4.1.a . . . . .	6
4.2	0.4.1.b . . . . .	6
<b>5</b>	<b>Evaluation</b>	<b>7</b>
<b>6</b>	<b>Conclusion</b>	<b>8</b>

# **1 Aims of the experiment**

The aim of this experiment is to understand the tools used in the electronics lab course. In order to do so, the termini of bandwidth and ramp-up time are introduced.

## 2 Preperational exercises

### 2.1 0.2.1.A

$$\begin{aligned}U(t) &= U_0 \cdot \sin(\omega t) \\U_{PP} &= 2 \cdot U_0 \\U_P &= U_0 \\U_{RMS} &= \frac{U_0}{\sqrt{2}}\end{aligned}$$

### 2.2 0.2.1.B

For a symmetrical rectangular voltage<sup>1</sup>

$$\begin{aligned}U_{RMS} &= \frac{U_0}{\sqrt{2}} \\&= 7.07 \text{ V}\end{aligned}$$

### 2.3 0.2.2.C

#### 2.3.1 0.2.2.C.1

$$\begin{aligned}\text{To proof: } R_i &= \frac{U_2 - U_1}{I_1 - I_2} \\U_n &= U_0 \frac{R_n}{R_n + R_i} \\I_n &= \frac{U_n}{R_n} \\\Leftrightarrow I_n &= U_0 \frac{1}{R_n + R_i} \\U_2 - U_1 &= U_0 \left( \frac{R_2}{R_2 + R_i} - \frac{R_1}{R_1 + R_i} \right) \\I_1 - I_2 &= U_0 \left( \frac{1}{R_1 + R_i} - \frac{1}{R_2 + R_i} \right) \\\Rightarrow \frac{U_2 - U_1}{I_1 - I_2} &= \frac{\left( \frac{R_2}{R_2 + R_i} - \frac{R_1}{R_1 + R_i} \right)}{\left( \frac{1}{R_1 + R_i} - \frac{1}{R_2 + R_i} \right)} \\&= \frac{R_2(R_1 + R_i) - R_1(R_2 + R_i)}{R_2 + R_i - R_1 - R_i} \\&= \frac{R_i(R_2 - R_1)}{R_2 - R_1} \\&= R_i\end{aligned}$$

---

<sup>1</sup>In this case with  $U_P = 10 \text{ V}$

### 2.3.2 0.2.2.C.2

$$\begin{aligned}U_0 &= 10 \text{ V} \\U_n(50 \Omega) &= 5 \text{ V} \\U_n &= U_0 \frac{R_n}{R_n + R_i} \\ \Rightarrow R_i &= 50 \Omega\end{aligned}$$

### 2.4 0.3.3.E

$$\begin{aligned}\text{To proof: } B\Delta t &= 0.35 \\B &= \frac{1}{2\pi\tau} \\\Delta t &= t(0.9U_0) - t(0.1U_0) \\\text{Decharging-function of a capacitor: } U(t) &= U_0 \exp\left(-\frac{t}{\tau}\right) \\\frac{0.1}{0.9} &= \exp\left(-\frac{\Delta t}{\tau}\right) \\\Leftrightarrow \Delta t &= -\ln\left(\frac{1}{9}\right) \tau \\&= 2.197\tau \\\Rightarrow B\Delta t &= \frac{2.197}{2\pi} \\\approx &0.35\end{aligned}$$

## 3 Procedure

### 3.1 0.4.1.a

Different signals at different frequencies and amplitudes shall be observed at the oscilloscope.

### 3.2 0.4.1.b

$\Delta t$  of a rectangular voltage shall be determined by measuring the delay from  $0.1U_0$  to  $0.9U_0$  with the oscilloscope.<sup>2</sup>

---

<sup>2</sup>We must also pay attention to the bandwidth of the oscilloscope which is - so says the manual - 60 MHz

## **4 Measurement**

**4.1 0.4.1.a**

**4.2 0.4.1.b**

## 5 Evaluation

## 6 Conclusion