

Electronics Lab Course

Experiment #0: Introduction and Preparational Experiment

Christopher Jörn

April 12, 2015

Contents

1	Aims of the experiment	2
2	Theoretical background	3
3	Preperational exercises	4
4	Experiment set-up	6
5	Procedure	7
6	Measurement	8
7	Evaluation	9
8	Conclusion	10

1 Aims of the experiment

2 Theoretical background

3 Preperational exercises

0.2.1.A

$$\begin{aligned}U(t) &= U_0 \cdot \sin(\omega t) \\U_{PP} &= 2 \cdot U_0 \\U_P &= U_0 \\U_{RMS} &= \frac{U_0}{\sqrt{2}}\end{aligned}$$

0.2.1.B

For a symmetrical rectangular voltage from U_P to $-U_P$ ¹

$$U_{RMS} = 0$$

0.2.2.C

$$\begin{aligned}\text{To proof: } R_i &= \frac{U_2 - U_1}{I_1 - I_2} \\U_n &= U_0 \frac{R_n}{R_n + R_i} \\I_n &= \frac{U_n}{R_n} \\\Leftrightarrow I_n &= U_0 \frac{1}{R_n + R_i} \\U_2 - U_1 &= U_0 \left(\frac{R_2}{R_2 + R_i} - \frac{R_1}{R_1 + R_i} \right) \\I_1 - I_2 &= U_0 \left(\frac{1}{R_1 + R_i} - \frac{1}{R_2 + R_i} \right) \\\Rightarrow \frac{U_2 - U_1}{I_1 - I_2} &= \frac{\left(\frac{R_2}{R_2 + R_i} - \frac{R_1}{R_1 + R_i} \right)}{\left(\frac{1}{R_1 + R_i} - \frac{1}{R_2 + R_i} \right)} \\&= \frac{R_2(R_1 + R_i) - R_1(R_2 + R_i)}{R_2 + R_i - R_1 - R_i} \\&= \frac{R_i(R_2 - R_1)}{R_2 - R_1} \\&= R_i\end{aligned}$$

¹In this case with $U_P = 10 \text{ V}$

0.3.3.E

4 Experiment set-up

5 Procedure

6 Measurement

7 Evaluation

8 Conclusion